

## **Lesson-1:**

A multimeter measures voltage, current, and resistance, essential for electronics. Using Ohm's law, it can help diagnose issues in circuits.

In multimeter, The black probe always connects to the common socket. The red probe must only be changed if you measure current. voltage and resistance is always the same socket now you can measure the resistance by just connecting one probe to one side of the resistor and the other probe to the other side of the resistor

- Ohm's law is the foundation of electronics, defining the relationship between voltage, current, and resistance. It's vital for understanding how these variables interact in circuits.
- Measuring voltage requires connecting the multimeter in parallel with the circuit. This technique helps determine whether power sources like batteries are functioning properly.
- Measuring current involves opening the circuit and connecting the multimeter in series. This method ensures accurate current readings but requires caution to prevent fuse damage.

## **Lesson-2:**

Learn how to control LED brightness using PWM (Pulse Width Modulation). By adjusting the duty cycle, you can dim various LEDs, including high-power ones, without wasting energy. By using an Arduino or a 555 timer chip to achieve this goal, making it accessible for all electronic enthusiasts.

Controlling LED brightness can be easily achieved using PWM (Pulse Width Modulation), which allows for efficient dimming without burning out the LEDs. This technique can be applied with or without microcontrollers like Arduino.

- Lowering the voltage beneath the forward voltage level reduces current consumption, thereby dimming the LED effectively. This approach prevents LED burnout and extends its lifespan.
- Using a potentiometer to control brightness may seem simple but is inefficient for high power LEDs, as it wastes energy and requires expensive components. A better alternative is PWM.
- PWM operates by rapidly switching the power to the LED on and off, creating a perceived dimming effect while maintaining constant voltage. This allows for precise control over brightness. To control LED brightness using PWM (Pulse Width Modulation), adjust the duty cycle for different brightness levels. It also introduces the 555 timer chip for simple signal generation.
- A higher duty cycle means brighter light, while a lower duty cycle dims the LED. This relationship shapes how we perceive light intensity.

## **Lesson-3:**

**ATtiny85** microcontroller is used to control a **WS2801 LED strip** with different animations, cycled using a push button. The **ATtiny85** is chosen over an **ATmega328** (found in an Arduino Uno) due to its affordability and sufficient IO pins. Since the **ATtiny85** cannot be directly programmed via Arduino, the video demonstrates how to program it using an **Arduino Uno as an ISP (In-System Programmer)**.

**Steps:**

### **1. Installing Required Software & Board Files:**

- Download and install **Arduino IDE v1.0.5** (not the **beta version**).
- Download ATtiny board data from **highlowtech.org** and place it in the Arduino hardware folder.

### **2. Uploading the Arduino ISP Sketch:**

- The **Arduino Uno** is prepared as an **ISP programmer** by uploading the **ArduinoISP** sketch.

### **3. Understanding ATtiny85 Pinout & Wiring:**

- **Pin 4 = GND, Pin 8 = VCC.**
- **IO Pins:** 2, 3, 5, 6, 7.
- Some pins support **analog input** and **PWM output**.
- **Wiring to Arduino Uno:**
  - **Arduino Pin 13 → ATtiny IO 2**
  - **Arduino Pin 12 → ATtiny IO 1**
  - **Arduino Pin 11 → ATtiny IO 0**
  - **Arduino Pin 10 → ATtiny Reset (Pin 1)**
  - **5V → ATtiny Pin 8 (VCC)**
  - **GND → ATtiny Pin 4 (GND)**
  - A **10µF capacitor** is placed between **Arduino Reset & GND** to prevent auto-reset.

### **4. Uploading a Simple LED Blink Sketch:**

- **ATtiny85 is programmed** via **Arduino ISP** with a 1 MHz clock.
- Error messages about **PAGE1** appear but don't affect functionality.

### **5. Building an ATtiny85 Programming Shield:**

- A **custom PCB shield** is made with **male headers** for easy ATtiny85 programming.

## 6. SPI Limitations & Bit-Banging Solution:

- ATtiny85 **does not support native SPI**, which is required for the **WS2801 LED strip**.
- A **bit-banging SPI library** from **SparkFun** is used to emulate SPI communication.

## 7. Project Status & Future Plans:

- **Testing ATtiny85 with WS2801 LEDs** was successful.
- Further development on **animations and programming improvements** will be shown in future videos.

### Conclusion:

The ATtiny85 is successfully programmed using an Arduino Uno, and a **custom PCB shield** makes the process easier. Though it lacks native SPI support, **bit-banging** allows communication with **WS2801 LEDs**, making the project viable.

- The Arduino's analog write function allows users to create PWM signals by varying voltage levels, demonstrating how to manipulate LED brightness effectively. A potentiometer is used to adjust this value.
- The 555 timer chip is highlighted as an easy alternative for generating PWM signals, allowing hobbyists to control duty cycles without complex setups. It can be wired simply for various projects.

## Lesson-4:

Using **Bluetooth module (HC-05)** with an **Arduino Nano** to wirelessly control an **RGB LED** via an **Android smartphone**.

### Key Topics Covered:

#### 1. Introduction to Bluetooth Module & Arduino Nano:

- The **HC-05 module** has **four pins** and easily connects to **Arduino projects**.
- The **Arduino Nano**, which is smaller but has the same microcontroller as the **Arduino Uno**, is used.

#### 2. Voltage Level Conversion:

- **Arduino uses 5V logic**, but the **Bluetooth module operates on 3.3V logic**.
- The module can receive **3.3V signals** from Arduino but sending **5V data** to the module can damage it.

- A **voltage divider** with a **2kΩ and 4.7kΩ resistor** is used to step down the voltage.

### 3. Wiring Connections:

- **Common anode RGB LED** is used, with three **cathodes** connected to **digital pins 8, 9, and 10** through **460Ω resistors**.
- **HC-05 Bluetooth module** is connected via **RX and TX pins**, using a **voltage divider for safety**.

### 4. Arduino Code:

- The code listens for specific **keywords** (e.g., "red," "green," "blue").
- When a keyword is received, the **corresponding LED color lights up**.
- Arduino also **sends a response** back to the smartphone via Bluetooth.
- Users can **modify the keywords** to control other devices.

### 5. Uploading the Code:

- **Before uploading, TX and RX connections** to the Bluetooth module must be **disconnected**, as they interfere with the upload process.
- After uploading, **reconnect the module** and **pair it** with the smartphone.
- Default **pairing codes** for HC-05 are **1234** or **0000**.

### 6. Final Testing & Demonstration:

- The **RGB LED successfully changes colors** based on **Bluetooth commands**.
- Arduino **responds with text confirmations**.

## Conclusion:

This tutorial shows how to use a **Bluetooth module** with **Arduino Nano** to control an **RGB LED wirelessly**. The project is simple, effective, and can be **extended to control other devices**. More creative applications can be built using this method.

## Lesson-5:

**TO control a large number of LEDs** (such as in a **4x4x4 RGB LED cube** or a **10x5 LED matrix**) using **multiplexing** and **LED driver circuits** while minimizing the number of **Arduino I/O pins** required.

### Key Topics Covered:

#### 1. The Problem – Limited I/O Pins:

- A **10x5 LED matrix** has **50 LEDs**, while a **4x4x4 cube** has **192 LEDs**.

- Even **Arduino Mega (54 I/O pins)** isn't enough to control them **individually**.

## 2. Solution – Multiplexing & LED Driver:

- **Multiplexing** allows controlling **multiple LEDs with fewer I/O pins**.
- The project uses:
  - **Arduino Nano**
  - **TLC5940 LED driver**
  - **5 p-channel MOSFETs (F9540N)**
  - **Resistors (1kΩ & 2kΩ)**

## 3. How Multiplexing Works:

- **Rows share anodes** (positive), and **columns share cathodes** (negative).
- When an **anode row is HIGH** and a **cathode column is LOW**, the LED lights up.
- To display **multiple LEDs**, each row is **turned on one by one** so fast that the human eye perceives it as a **steady image**.
- This method is called **Persistence of Vision (POV)**.

## 4. Challenges in Multiplexing:

- **Multiple LEDs can create unwanted connections**, lighting unintended LEDs.
- Solution: **Light up each row one at a time** in rapid succession.

## 5. Hardware Setup:

- **P-channel MOSFETs** are used to **switch anode rows ON/OFF** since the Arduino **can't supply enough current directly**.
- **TLC5940 LED driver** controls the **cathode columns** and manages current flow.
- **Resistors** help set current limits and prevent damage.

## 6. Wiring the Circuit:

- **MOSFET connections:**
  - **Source → 5V**
  - **Drain → Anode Rows**
  - **Gate → Arduino I/O Pins (4-8)**
  - **Pull-up resistors (1kΩ) between Gate & 5V**
- **TLC5940 connections:**
  - **Pin 28 → Column 1, Pin 1 → Column 2, Pin 2 → Column 3** (and so on).

- A **2kΩ resistor** sets **constant current** for LEDs (20mA per LED).

## 7. Coding the Arduino:

- **TLC5940 Arduino Library** simplifies control.
- The code handles:
  - **Row switching** using **MOSFETs**.
  - **LED brightness control** with **TLC5940**.
  - **Animations** like a **sine wave**, **moving text (E)**, and **static patterns**.

## 8. Testing & Results:

- Initially, a **moving sine wave** is displayed.
- Adjusting the **row switching speed** reveals **individual row illumination**.
- The final effect creates a **smooth animation**.

## 9. Future Applications:

- The same **multiplexing technique** will be used in an **RGB LED cube** in an upcoming video.

## Conclusion:

To control large LED setups efficiently using **multiplexing**, **MOSFETs**, and **LED drivers**. The technique can be applied to **LED cubes**, displays, and animations.

## Lesson-6:

To use an **ATmega328P microcontroller** without an Arduino board, embedding it directly into a circuit for a more **compact and permanent solution**.

### Key Topics Covered:

#### 1. The Problem – Arduino Boards Are Too Big

- You've built a **cool circuit** (e.g., an **LED color organ**).
- Breadboards are **temporary solutions**.
- Arduino **shields** work, but for a more **compact build**, you need something smaller.
- The **ATmega328P** (the chip inside an Arduino Uno) is **too large for small gadget boxes**.

#### 2. The Solution – Freeing the ATmega328P

- **Remove** the ATmega328P from the Arduino Uno.
- **Embed it directly into your circuit** on a breadboard or PCB.

### 3. Required Components

Component	Function
<b>ATmega328P</b>	The microcontroller (brain of the Arduino)
<b>16 MHz Crystal</b>	Provides an external clock signal
<b>Two 22pF Capacitors</b>	Stabilizes the crystal oscillator
<b>10kΩ Resistor</b>	Pull-up resistor to prevent unwanted resets
<b>5V Power Supply</b>	Powers the microcontroller

### 4. Wiring the ATmega328P

- **Power:**
  - Pin 7, 20, 21 → 5V
  - Pin 8, 22 → Ground
- **Clock Signal (External 16 MHz):**
  - Crystal connects to Pins 9 & 10
  - Each capacitor (22pF) connects from crystal pins to ground
- **Reset Circuit:**
  - 10kΩ resistor between Reset Pin (1) and 5V to prevent accidental resets

#### Alternative:

- If you **don't need 16 MHz**, the ATmega328P has an **internal 8 MHz oscillator**, but you must **burn a new bootloader**.

### 5. Downsides of Removing the Arduino Board

Missing Feature	Consequence
<b>Reset Button</b>	Must manually wire one
<b>Only 5V Input</b>	No onboard voltage regulator
<b>No USB-to-Serial Conversion</b>	Needs an external programmer for code upload
<b>No Short-Circuit or Overvoltage Protection</b>	Risk of damaging the chip

If you **understand the risks**, these missing features **won't be a big problem**.

## 6. Finding the Correct ATmega328P Pins

- The pin numbers on the ATmega328P don't match the Arduino digital pin numbers.
- Example:
  - Arduino Digital Pin 9 → ATmega328P Pin 15
  - Arduino Digital Pin 10 → ATmega328P Pin 16
  - (Follow the ATmega328P pinout diagram for mapping)

## 7. Uploading Code to the ATmega328P

### Method 1: The Lazy Way (Swap the Chip)

1. Remove the ATmega328P from your breadboard.
2. Plug it into the Arduino Uno.
3. Upload the code normally.
4. Remove and place it back in your circuit. ↗
5. Downside: Annoying and not practical.

### Method 2: Using an Arduino as a Programmer

1. Connect Arduino to ATmega328P:
  - Arduino TX (Pin 1) → ATmega Pin 3
  - Arduino RX (Pin 0) → ATmega Pin 2
  - Arduino Reset → ATmega Pin 1
2. Remove the Arduino's own ATmega chip (if it's removable).
3. Upload code as usual in the Arduino IDE.

### Method 3: Using an FTDI USB-to-Serial Converter

1. Connect an FTDI module:
  - RX → TX
  - TX → RX
  - Reset → Reset
2. Upload code normally using the Arduino IDE. ↗
3. Advantage: No need to use an Arduino board.

### Method 4: ICSP (In-Circuit Serial Programming)

- Requires an **ICSP programmer** and extra software.
- More complex but useful for advanced projects.

## 8. Finalizing the Circuit

- Once everything works on the **breadboard**, solder the circuit onto a **PCB**.
- **Add female headers for RX/TX** to allow future reprogramming.
- **Now, you have a standalone Arduino!**

## 9. Conclusion

- You can **remove the ATmega328P from the Arduino Uno** and use it independently.
- This **saves space** and allows for **custom enclosures**.
- Programming can be done using **Arduino, FTDI, or ICSP**.

 **Tip:** If you don't need USB communication, this is a **cheap way** to use an **Arduino in final projects!**

# Lesson-7:

## 7-Segment Display with and Without Arduino

### 1. Introduction

- 7-segment displays are old-school but useful for simple output projects (clocks, temperature sensors, power meters).
- Can be controlled **with** or **without** a microcontroller.

### 2. Types of 7-Segment Displays

- **Single-digit** vs. **multi-digit** displays.
- **Common anode** (shared positive terminal) and **common cathode** (shared negative terminal).
- Each segment is labeled **A to G + DP (decimal point)**.

### 3. Controlling a 7-Segment Display Without a Microcontroller

- Uses a **BCD to 7-segment driver** (SN74LS247).
- **Connection Details:**
  - Pins A-G connect to driver IC.
  - Common anode to **5V**.
  - **220Ω resistors** limit LED current.
- **Functionality:**

- IC converts **4-bit binary (ABCD)** to display numbers.
- Example: A=low, B=high, C=high, D=low → displays '6'.

#### **4. Binary Counter for Automatic Number Display**

- Uses **SN74290 4-bit binary counter**.
- Counts automatically when clocked.
- Possible applications:
  - **Manual counter (push button)**.
  - **Tilt switch or sensor-based counter**.

#### **5. Multiplexing for Multi-Digit Displays**

- Multi-digit displays **share LED segments** but have **separate anodes**.
- **Multiplexing Technique:**
  - Controls multiple digits with fewer pins.
  - Activates one digit at a time in rapid succession.

#### **6. Using Arduino with an I<sup>2</sup>C Display Driver (SAA1064)**

- **SAA1064 IC** can handle **4-digit displays** via **I<sup>2</sup>C**.
- **Connections:**
  - **Pin 23 → A4 (SDA), Pin 24 → A5 (SCL)** (with 4.7kΩ pull-ups).
  - **NPN transistors (BC337)** for digit selection.
- **Code & Library:**
  - Uses **SAA1064 library** for easy control.
  - Reduces Arduino pin usage and processing load.

#### **7. Key Takeaways**

- **Without Arduino:** Use **BCD driver + binary counter** for simple counters.
- **With Arduino:** Use **multiplexing** or **I<sup>2</sup>C-based drivers** for multi-digit displays.
- **Experimentation:** Try different **libraries and ICs** to optimize performance.

## **Lesson-8:**

### **Notes on 7-Segment Display & Arduino Clock**

#### **Introduction**

- 7-segment displays are useful for small projects like clocks, temperature sensors, and power supply meters.
- They can be used with or without an Arduino.

### Types of 7-Segment Displays

- Single-digit, two-digit, and multi-digit displays exist.
- Always check the datasheet for pin configurations.
- Example: LTS546AG – has 8 LEDs (7 segments + 1 decimal point) with a common anode configuration.

### Controlling Without a Microcontroller

- **BCD to 7-segment display driver (SN74LS247)**: Converts binary-coded decimal (BCD) to segment signals.
- **Binary counter (SN74290)**: Generates BCD outputs for counting applications.

### Multiplexing for Multi-Digit Displays

- Required because a microcontroller has limited output pins.
- Uses 8 segment pins and 4 common anode pins.
- Reduces pin usage but requires rapid switching.

### Using an I<sup>2</sup>C Display Driver (SAA1064)

- Controls up to 4 digits efficiently using I<sup>2</sup>C protocol.
- Requires pull-up resistors and transistors for multiplexing.
- Saves Arduino processing power.

### Code Implementation

- Uses an SAA1064 library for easy integration.
- Example code allows displaying numbers with minimal CPU usage.

### Notes on Proper LED Handling

#### Basic LED Circuit

- **Parameters to check:** Forward voltage (e.g., 3.2V), ideal current (e.g., 20mA).
- **Resistor Calculation:**
  - **Using Ohm's Law:**  $R = \frac{V}{I}$
  - Example: For a 9V battery and LED with 3.2V forward voltage:
    - Resistor voltage drop = 9V - 3.2V = 5.8V

- $R = \frac{V}{I} = \frac{5.8V}{0.02A} = 290\Omega$  (nearest higher available value:  $300\Omega$ ).
- **Power Rating of Resistor:**  $P=V\times I$ 
  - Example:  $5.8V \times 0.02A = 0.116W$
  - Use a  $\frac{1}{4}$  watt resistor ( $0.25W$ ) for safety.

## Using Multiple LEDs

- **Parallel connection** (each LED has its own resistor) wastes power.
- **Series connection:** Reduces wasted power by sharing a single resistor.
- **Limitation:** Total LED voltage should not exceed power supply voltage.

## Advanced Considerations

- **Forward Voltage Variation:**
  - Manufacturer specifications can be inaccurate.
  - Small voltage changes cause large current variations.
  - Solution: Use a small resistor to stabilize current.
- **Parallel LED Issue:**
  - LEDs have slightly different forward voltages, causing uneven brightness and faster degradation.
  - Solution: Use separate resistors for each LED.

## Constant Current Driving

- **Best method:** Use a constant current source instead of constant voltage.
- **Example circuits:**
  - **LM317 with resistor** (simple but inefficient).
  - **Dedicated LED drivers (e.g., TLC5940)** for high-efficiency applications.

## Conclusion

- Always use resistors for LED protection.
- Prefer series over parallel connections to save power.
- Use constant current drivers for long-lasting LEDs.
- Balance effort vs. benefit based on project complexity.

## Lesson-9:

## **Diodes & Their Applications**

### **1. Introduction to Diodes**

- Diodes are found in power supplies, consumer electronics, and circuit boards.
- They allow current to flow in one direction only.

### **2. Diodes in DC Circuits (Polarity Protection)**

- If power is connected in reverse, circuits can get damaged.
- A diode prevents reverse current flow, protecting the circuit.
- **Voltage Drop Issue:**
  - Example: A **1N4007** diode drops around **0.65V**, reducing supply voltage.
  - Causes power loss, which increases with higher current.
  - Large loads require diodes with higher current ratings.

### **3. Diodes in AC Circuits (Rectification)**

- **AC to DC Conversion:**
  - AC alternates polarity; diodes allow only positive voltage through.
  - **Half-Wave Rectification:** A single diode removes negative cycles, producing pulsating DC.
  - **Adding a Capacitor:** Smooths the voltage, but still fluctuates under load.
- **Bridge Rectifier (Full-Wave Rectification):**
  - Uses four diodes to convert both positive and negative cycles into DC.
  - Allows more efficient power conversion.
  - Circuit diagram explanation:
    - Current flows differently depending on AC polarity but always outputs DC.

### **4. Conclusion**

- Diodes are essential for circuit protection and AC to DC conversion.
- Different types of diodes exist for specific applications.
- Understanding voltage drop, current rating, and rectification is key to proper diode usage.

## **Lesson-10:**

### **Digital-to-Analog Converters (DACs)**

## 1. Introduction to DACs

- Converts **digital signals (binary: 0s and 1s)** into **analog signals** (continuous waveforms like sine, triangle, or ramp).
- Used in audio systems, frequency generators, and other applications requiring analog output.

## 2. DAC Techniques & Resolution

- **R-2R Ladder DAC:**
  - Uses resistors in a voltage divider network.
  - Example circuit using **Arduino Nano** digital pins and **10kΩ & 20kΩ resistors**.
  - Voltage output depends on digital input value (e.g., 200 → ~3.8V output).
  - Resistor tolerance affects precision.
- **Generating Analog Waveforms:**
  - **Ramp Function:** Gradually increases from 0 to max and resets.
  - **Triangle Wave:** Increases and decreases repeatedly.
  - **Sine Wave:** Can be generated for smooth audio signals.

## 3. Using DAC with a Speaker

- Direct connection to a resistor ladder **fails** as the voltage drops due to load.
- Solution: Use an **Op-Amp as a Voltage Follower** to stabilize the output.
- Generates signals between **200Hz and 3kHz**, similar to Atari 2600 sound effects.

## 4. Alternative DAC Methods

- **IC-based DACs:** More precise, compact, and efficient.
  - Example: **DAC0800, PCF8591 (8-bit), MCP4725 (12-bit)**.
- **PWM (Pulse Width Modulation) as DAC Alternative:**
  - **Arduino analogWrite() function** produces PWM output.
  - PWM duty cycle determines average voltage (e.g., 200 → ~3.8V output).
  - Needs **Low-Pass Filter (LC filter)** to smooth out the signal.

## 5. Applications & Future Projects

- **Audio processing, frequency generation, and analog signal synthesis.**

- Can be used in Arduino projects for **audio effects, music synthesis, and communication systems.**

## Lesson-11:

### TC35 GSM Module to send SMS with Arduino UNO

#### 1. Introduction to TC35 GSM Module

- A **GSM (Global System for Mobile Communications) module** used for **sending SMS** via a microcontroller.
- Requires a **SIM card** (preferably prepaid) for sending messages.

#### 2. Hardware Setup

- **SIM Card Insertion:**
  - Unlock the SIM using a smartphone before inserting it into the module.
- **Powering the Module:**
  - Supports **5V or 12V power supply**.
  - **Caution:** The onboard **MAX232 IC (RS232 converter)** operates on **max 6V, so avoid 12V unless you remove MAX232**.
- **Startup Process:**
  - Requires pressing a **button** to connect to the network.
  - To automate this, connect the **right side of the button to Arduino Pin 10**.
  - When **Pin 10 is pulled LOW**, the login process starts.

#### 3. Connecting TC35 to Arduino

- **FTDI Serial Communication:**
  - **TX → TXD0, RX → RXD0, GND → GND** (labeling is reversed on the board).
  - Works with both **3.3V and 5V logic levels**.
- **Arduino Serial Monitor Setup:**
  - Baud rate: **9600**
  - Line Ending: **Carriage Return**

#### 4. Sending SMS using AT Commands

- **Basic AT Commands:**
  - AT → Response: OK (indicates the module is working).

- AT+COPS? → Shows **network operator**.
- AT+CSQ → Shows **signal strength**.
- **Sending SMS:**
  - Enter SMS text and finish with a **DOT (.) at the end**.
  - Uses the **sendTextMessage()** function in the Arduino code.
  - Modify the **recipient phone number** in the

## 5. Applications & Future Enhancements

- **GSM-based Alarm System:** Sends an SMS alert when triggered.
- **Home Automation:** Remote control via SMS commands.
- **IoT Applications:** Wireless data transmission.
- **Further Improvements:**
  - Use **external power source** for stability.
  - Add **error handling** for failed SMS transmissions.

# Lesson-12:

## Inductors and Their Importance in Electronics

### 1. Introduction to Inductors

- Inductors (coils) are fundamental **passive components** in electronics, along with **resistors** and **capacitors**.
- Found in **motors, transformers, relays**, and many other applications.
- Function based on the **relationship between current and magnetic fields**.

### 2. Basic Principle of Inductors

- **Current Flow → Magnetic Field Formation**
  - When current flows through a wire, it generates a **magnetic field** around it.
  - **Higher current** produces a **stronger magnetic field**.
  - Example: **Current probe** can measure this field and convert it to current values.
- **Induced Voltage (Electromagnetic Induction)**
  - A **changing magnetic field** induces a voltage in a conductor.
  - Examples: **AC motors, DC motors, transformers**.

- The **mains electricity** in walls induces a small voltage in human bodies because we act as antennas.

### 3. Enhancing Magnetic Fields with Coils

- **Plain wires** create weak magnetic fields.
- **Winding the wire into a coil** increases magnetic force.
- **Adding a ferromagnetic core (iron core)** significantly boosts the field.
- **Applications:**
  - **Electromagnets:** Used in **relays** to switch high-power circuits.
  - **Transformers:** Use two coils to **transfer power** between circuits.
- **Inductance (L):**
  - **Measured in Henry (H).**
  - Depends on **coil dimensions, number of turns, and core material.**
  - Measured using an **RLC meter** or calculated through experiments.

### 4. Behavior of Inductors in DC Circuits

- **DC voltage can only switch ON or OFF.**
- **Current Delay Effect:**
  - In a **resistor-LED circuit**, current follows the voltage immediately.
  - In an **inductor-LED circuit**, current takes time to **reach its final state**.
  - More inductance → **slower response**.
- **Lenz's Law:**
  - **An induced current always opposes the change that created it.**
  - **When current starts**, the inductor **resists it**.
  - **When current stops**, the inductor **pushes energy back** into the circuit.
  - This effect is used in **boost converters** and **motor control circuits**.

### 5. Applications of Inductors

- **Boost Converters** (e.g., 3.7V battery → 5V output):
  - Store energy in the magnetic field when the switch is **closed**.
  - Release energy when the switch is **open**, increasing output voltage.
- **Motor Control (PWM Switching):**

- Motors are made of **coils**, so they can create **high voltage spikes** when turned off.
- **Flyback Diodes** protect transistors from these voltage spikes.
- **Switching Power Supplies (Step-Down Converters):**
  - Inductors **smooth the output voltage** by acting as energy storage.

## 6. Next Steps (AC Circuits & Frequency Filters)

- Inductors behave **differently in AC circuits**.
- They are used in **frequency filters, impedance matching, and signal processing**.

# Lesson-13:

## Inductors in AC Circuits & Reactance

### 1. Introduction to Inductive Reactance

- In **AC circuits**, inductors behave **differently** compared to DC circuits.
- **New Concept: Reactance (XL)**
  - Unlike resistors, **inductors oppose current flow using a magnetic field** rather than converting power into heat.
  - **Reactance (XL) is the frequency-dependent "resistance" of an inductor.**

### 2. Experiment: Inductor Protecting an LED

- A **230V to 15V transformer** powers an LED.
- Without an inductor → **LED burns instantly**.
- Adding a **1H inductor** in series → LED lights up **safely**.
- **Why?**
  - The inductor **limits current flow** by increasing reactance at high frequencies.
  - If replaced with a  **$33\Omega$  resistor**, the LED would still burn, proving that inductance itself **limits current differently from resistance**.

### 3. Understanding Inductive Reactance ( $X_L$ )

- **Ohm's Law Still Applies:**
  - **Less reactance → More current flow**
  - Example: **Opening the iron core of the inductor decreases reactance → Current increases.**
- **Reactance Depends on Frequency**

- **Higher Frequency → Higher Reactance → Lower Current**
- Experiment: Increasing frequency from **50Hz** → **10kHz** makes the LED dimmer.
- **Formula for Inductive Reactance:**  $X_L = 2\pi f L$ 
  - $X_L$  = Inductive reactance (Ohms,  $\Omega$ )
  - $f$  = Frequency (Hz)
  - $L$  = Inductance (Henrys, H)
- **Applications of Reactance:**
  - **Power grids & transformers** must manage reactance to reduce energy loss.
  - **Reactance-based circuits** help in frequency filtering.

#### 4. Inductors in Frequency Filters

- **Inductors act as frequency-dependent resistors**, allowing specific signals to pass.
- **Types of Filters:**
  - **High-Pass Filter** → Blocks low frequencies, allows high frequencies.
  - **Low-Pass Filter** → Blocks high frequencies, allows low frequencies.
- **Simulation in LTspice:**
  - **With a  $5k\Omega$  resistor**, a **high-pass filter** blocks frequencies **below 800Hz**.
  - A **low-pass filter** blocks frequencies **above 800Hz**.
- **Real-world use:**
  - Audio circuits: **Extract bass or treble**.
  - Power supplies: **Reduce noise & stabilize voltage**.

#### 5. Phase Shift in AC Circuits

- In AC circuits, **voltage and current are not always in sync**.
- **Phase Shift ( $\Phi$ )**
  - With a pure resistor, voltage and current are **in phase**.
  - With an inductor, **current lags behind voltage** by up to  **$90^\circ$** .
- **Practical Example:**
  - **Microwave motor** → Creates a  **$36^\circ$  phase shift**, proving it behaves like an inductive load.

- **Transformer circuit with an inductor** → Phase shift changes based on the iron core position.
- **Measuring phase shift** helps determine inductance in **power grids & circuits**.

## 6. Measuring Inductance & Alternative Tools

- **RLC meters** are expensive.
- **Affordable alternative: Transistor Tester (~\$20 on Amazon/eBay)**
  - Measures **inductance, resistance, capacitance, and transistor gain**.
  - Works well for **large coils**, but struggles with **small inductors (<100µH)**.
  - Based on a **German microcontroller project** → Reliable and useful.

## 7. Conclusion

- **Inductive reactance ( $X_L$ ) depends on frequency and limits current flow.**
- Inductors create phase shifts and are used in power grids, motors, and filtering circuits.
- Practical applications include AC motors, power supplies, audio circuits, and energy-efficient transformers.
- Low-cost tools like transistor testers help measure inductance accurately.

# Lesson-14:

## Understanding Capacitors in Circuits

### 1. Introduction to Capacitors

- **Common Issue:** If your **monitor or TV stops working**, faulty **capacitors** could be the reason.
- **Capacitors are everywhere** in consumer electronics, playing **vital roles in circuit operation**.

### 2. What is a Capacitor?

- A capacitor stores electrical energy using two **conductive plates** separated by an **insulating material (dielectric)**.
- **Basic Experiment:**
  - Using **two aluminum plates** placed **close together** → forms a simple capacitor.
  - **Connecting it to a 30V power source** → electrons accumulate on one plate, creating an **electrostatic field**.

- The capacitor **briefly allows current flow**, then stops as it becomes fully charged.

### 3. Factors Affecting Capacitance (C)

- **Capacitance (C) depends on:**
  - **Plate area (A)** → Larger plates = Higher capacitance.
  - **Distance between plates (d)** → Smaller distance = Higher capacitance.
  - **Dielectric material** → Using distilled water or specialized insulators can increase capacitance.
- **Capacitor Formula:**  $C=\epsilon A/d$ 
  - **C** = Capacitance (Farads, F)
  - **$\epsilon$**  = Dielectric permittivity
  - **A** = Plate area
  - **d** = Distance between plates

### 4. Real-World Capacitors

- **Electrolytic Capacitors:**
  - Made from **thin metal films** with a **dielectric layer**.
  - **Polarity matters!** Reversing connections can damage them.
  - **Voltage Rating:** Exceeding the voltage limit can **cause failure** due to dielectric breakdown.

### 5. Capacitor Behavior in Circuits

- **DC Circuits:**
  - **Capacitors act like temporary batteries** → Charge and discharge energy.
  - Used for **voltage smoothing & noise reduction** in power supplies.
- **AC Circuits:**
  - **Capacitors oppose current flow** at high frequencies → This effect is called **Capacitive Reactance (XC)**.
  - **Formula for Capacitive Reactance:**  $X_C=1/2\pi fC$ 
    - **Higher frequency = Lower reactance** (easier for AC to pass).
    - **Lower frequency = Higher reactance** (harder for AC to pass).

### 6. Practical Applications

- **RC Filters (Capacitor + Resistor):**
  - **High-pass filters** allow **high frequencies** to pass while **blocking low frequencies**.
  - **Low-pass filters** allow **low frequencies** to pass while **blocking high frequencies**.
  - **Used in audio processing & signal conditioning.**
- **Power Factor Correction:**
  - **Inductive loads (motors, transformers) cause phase shift** → results in **reactive power loss**.
  - **Solution:** Adding **capacitors in parallel** to **cancel the phase shift**, improving **power efficiency**.

## 7. Conclusion

- **Capacitors store energy & manage current flow in circuits.**
- **Used for filtering, power supply stability, and reactive power compensation.**
- **Understanding capacitance helps in designing efficient circuits & troubleshooting electronics.**

# Lesson-15:

## Understanding Temperature Measurement & DIY Thermometer

### 1. Importance of Temperature Measurement

- Essential for **3D printing (nozzle & bed temperatures)** and various **industrial applications**.
- Measuring **accurate temperatures** is more **challenging** than it seems.

### 2. Temperature Sensors: NTC vs. PT100

#### NTC Thermistors (Negative Temperature Coefficient)

- **Resistance decreases as temperature increases.**
- Available in **different nominal values** (e.g., **1KΩ, 10KΩ, 100KΩ** at 25°C).
- **Issues:**
  - **Non-linear response.**
  - **Limited precision** (used in low-cost applications).
  - **Max temperature ~150°C.**

#### PT100 (Platinum Resistance Thermometer - RTD)

- Resistance increases as temperature rises.
- Nominal resistance =  $100\Omega$  at  $0^\circ\text{C}$ .
- More linear than NTC thermistors → better accuracy.
- Temperature range: up to  $850^\circ\text{C}$ .
- Requires constant current ( $\sim 1\text{mA}$ ) for accurate measurement.

### 3. Measuring Temperature Using PT100

- Using Ohm's Law ( $V = IR$ ), measure resistance to determine temperature.
- Challenges:
  - Offset voltage at  $0^\circ\text{C}$  affects accuracy.
  - Low voltage signals need amplification.

#### Solutions:

1. Using a Voltage Divider + Op-Amp (Differential Amplifier)
  - Subtracts offset voltage for more accurate readings.
2. Wheatstone Bridge Circuit
  - Uses balanced resistors to measure small resistance changes.
  - More stable and minimizes errors.
3. Amplification with a Non-Inverting Op-Amp
  - Increases small voltage changes for better measurement.

### 4. Using a Pre-Made PT100 Transmitter

- Easier alternative: Industrial PT100 Transmitter ( $\sim \$5$  cost).
- Converts resistance changes into a 4-20mA current signal.
- Advantages:
  - More accurate ( $\sim 0.2\%$  error).
  - Works in 2-wire or 3-wire configurations (compensates wire resistance).

#### Connecting the Transmitter:

- Power: 24V supply in series with a  $250\Omega$  resistor.
- Output Signal:
  - $4\text{mA} \rightarrow -50^\circ\text{C}$
  - $20\text{mA} \rightarrow 150^\circ\text{C}$

- Convert **current to voltage** for microcontroller input.

## 5. DIY Thermometer with Microcontroller & LCD

- **Components:**
  - **16x2 LCD display** (for temperature output).
  - **Microcontroller (Arduino, ESP, etc.).**
  - **Analog pin to read voltage drop** across resistor.
- **Software Implementation:**
  - Read **10-bit ADC** voltage.
  - Map voltage to **temperature range**.
  - Display **temperature on LCD**.

## 6. Alternative IC-Based Temperature Sensors

### LM35 (Analog Sensor)

- **Linear output:** 0–1.5V for 2°C to 150°C.
- **Accuracy:** ±0.5°C.

### DS18B20 (Digital Sensor - 1-Wire Interface)

- Sends **temperature data digitally** (no need for ADC).
- **Accuracy:** ±0.5°C.

## 7. Limitations of Resistance-Based Sensors

- **Slow response time** due to **thermal inertia**.
- Other faster methods exist (e.g., thermocouples, infrared sensors) → topic for another video.

## Conclusion

- NTC thermistors are simple but **non-linear**.
- PT100 provides **high accuracy**, but requires **amplification & compensation**.
- Pre-made PT100 transmitters simplify measurement.
- IC-based sensors (LM35, DS18B20) offer easier alternatives.

## Lesson-16:

### Resistors

- **Resistors in Simple Circuits:** Without a resistor, components like LEDs can burn out due to excess current.
- **Ohm's Law for Calculation:** It explains how to use **Ohm's Law** to calculate the value of the resistor needed to prevent damage.  $V=IR$
- **High-Power Components:** When powering components that require more current, like high-power LEDs, the power rating of resistors is also crucial. **power resistors** are used to handle higher power ratings to avoid overheating.
- **Voltage Divider:** how resistors can be used in series to create a **voltage divider**, which allows you to get different voltage levels from a single supply voltage. This is useful, for example, in converting Arduino 5V signals to 3.3V for components like the ESP8266 Wi-Fi module.
- **Potentiometers:** Potentiometers are explained as variable resistors with a movable pin. They are used for adjusting voltage levels in circuits, such as adjusting inputs to microcontrollers or op-amps.
- **Pull-Up and Pull-Down Resistors:** These resistors are used to ensure stable logic levels in microcontrollers. **Pull-down resistors** pull the input to ground (0V), while **pull-up resistors** pull the input to +5V. This technique stabilizes inputs from switches or transistors.
- **Current Measurement (Shunt Resistors):** **Shunt resistors** are used to measure current in a circuit. A differential amplifier is used to amplify the voltage drop across the resistor, allowing for current calculation.
- **Other Uses of Resistors:** Resistors can also serve as **fuses** for circuit protection, **photoresistors** for light detection, **PT100** sensors for temperature measurement, and **strain gauges** for measuring weight.
- **AC Behavior:** Unlike inductors and capacitors, resistors don't produce a phase shift in **Alternating Current (AC)** circuits. However, as the frequency increases, resistors begin to consume more current. This is due to **parasitic capacitance** in the resistor itself, which lowers the overall impedance.
- **Conclusion:** The video wraps up by noting that real-world components have imperfections such as parasitic capacitance and inductance, which must be considered when designing circuits to prevent errors.

## Lesson-17: Oscillators

- **Introduction to Oscillators:** The video introduces the concept of oscillators, which are electronic circuits that generate periodic voltage signals (like square, triangle, or sine waves). These are used in devices for clock signals or data transmission.
- **Relaxation Circuits with RC Components:** The first oscillator discussed is the **astable multivibrator**. It uses two capacitors (C1 and C2) that alternate charging

through a resistor to a threshold voltage, triggering a transistor to discharge one capacitor while the other charges. This creates a square waveform. The frequency can be adjusted by changing the resistance or capacitance.

- **555 Timer:** The **555 timer** IC is introduced as another popular oscillator. It uses two comparators, logic gates, and an RS flip-flop. With a few components like capacitors and resistors, a variable frequency square wave can be created by charging and discharging a capacitor.
- **LC Tank Circuits:** **LC resonators** or tank circuits are used to create high-frequency oscillations. The capacitor charges and discharges through an inductor, creating a resonant frequency where the energy oscillates between the capacitor and inductor. This creates high-frequency waves, but parasitic resistance limits the duration of the oscillations.
- **Amplification of the Signal:** To maintain continuous oscillations, the energy from the LC tank circuit is fed into an amplifier (like an NPN transistor). The right amplification factor ensures a stable high-frequency output (e.g., a megahertz sine wave).
- **Crystal Oscillators:** For more stable and precise frequencies, **crystal oscillators** are used. These oscillators rely on the mechanical vibrations of a piezoelectric crystal, producing stable frequencies like a 16 MHz signal commonly used for microcontroller clocks.
- **Conclusion:** The video wraps up by highlighting the importance of oscillators in electronics, from simple RC circuits to advanced crystal oscillators, for generating stable, periodic signals used in various applications.

## Lesson-18: DC motors and ESCs (Electric Speed Controllers)

- **Introduction:** The video explores the workings of brushless **DC motors and ESCs (Electric Speed Controllers)**, which are used in various applications like electric longboards, quadcopters, and hard drives.
- **DC Motors:** DC motors have a rotor with coils connected to a commutator, which uses carbon brushes to reverse the magnetic polarity of the coils, generating rotational movement. This setup works by using direct current to create opposing magnetic fields, causing the rotor to turn.
- **Brushless DC Motors:** **Brushless motors** use a similar principle but without brushes. Instead, they use permanent magnets on the rotor and coils on the stator. The motor's rotor is energized in stages, creating a rotating magnetic field that drives the rotor. The commutator in DC motors is replaced by an **ESC** (electronic speed controller), which applies a control voltage to the coils in a specific sequence.
- **ESC Operation:** The ESC applies a voltage to the motor's coils in a specific order to create rotation. The frequency at which the six steps repeat determines the rotor's

speed (RPM). The higher the frequency, the higher the RPM. ESCs use **MOSFETs** (metal-oxide-semiconductor field-effect transistors) to switch the coils' states (high, low, or floating). The number of MOSFETs affects how much current the motor can handle, influencing its power and performance.

- **Motor Performance:** The video discusses how the **torque** and **RPM** of a brushless motor depend on factors like the number of coils and magnets. **Outrunner motors** (with magnets on the outside) have higher torque because they can accommodate more magnets, resulting in a lower RPM and higher torque for the same frequency.
- **KV Rating:** The **KV rating** of a motor indicates its RPM per volt applied. For example, a 520 KV motor at 7.4V reaches 3,750 RPM, while at 11.1V it reaches 5,644 RPM. A higher KV motor provides more RPM, but motor performance is not solely dependent on voltage. The ESC's frequency and the motor's properties also play significant roles in determining performance.
- **Conclusion:** The video concludes by summarizing how brushless motors and ESCs work, emphasizing the importance of voltage, frequency, and the motor's characteristics in achieving desired performance.

## Lesson-19: I<sup>2</sup>C (Inter-Integrated Circuit)

- **Introduction:** The video introduces the **I<sup>2</sup>C (Inter-Integrated Circuit)** protocol, a popular two-wire communication system used for connecting master devices (like a Wio Nano) to multiple slave devices. It is often used in projects like real-time clocks, PWM pins, and FM radio receivers. The video focuses on using I<sup>2</sup>C with an **Arduino** and a **TEA5767 FM radio IC**.
- **Building the Circuit:** Before connecting the I<sup>2</sup>C device to the master (Arduino), the presenter creates a **breakout board**. This involves preparing a strip board, adding headers, and connecting the necessary components (e.g., ground, 5V, antenna, audio output) to the radio IC. The **I<sup>2</sup>C SDA** (Serial Data) and **SCL** (Serial Clock) lines are connected to the **A4** and **A5** pins of the Arduino, respectively. Pull-up resistors ( $10k\Omega$ ) are added to the I<sup>2</sup>C lines to ensure stable voltage states for proper communication.
- **Sending Data:** Once the hardware is set up, the presenter explains how I<sup>2</sup>C communication works. It begins with a **start condition** (SDA goes low while SCL stays high). The **address** of the slave device is sent, followed by the **RW (Read/Write)** bit. Depending on whether the master wants to read or write, the Arduino sends the corresponding data bits. The **acknowledge bit** is sent by the slave to confirm readiness for the next data byte.
- **Configuring the Radio:** The first two bytes of data define the **PLL (Phase-Locked Loop)** value, which sets the frequency for the radio. For instance, to tune to a frequency of 95.6 MHz, the value is calculated (11,697) and converted into binary or

hexadecimal. After preparing the data, the transmission is finalized with a **stop bit**, and the Arduino can tune the radio.

- **Testing the Setup:** The presenter successfully tunes the radio and listens to the station. Due to low volume, an **amplifier and speaker** are used to hear the audio more clearly. An **oscilloscope** is recommended to observe the I<sup>2</sup>C communication and decode the data bits. The clock frequency is 100 kHz.
- **I<sup>2</sup>C Read Function:** After confirming the data transmission, the presenter writes a function to **read** data from the I<sup>2</sup>C device. The process is similar, but this time the master stores the received data in a buffer for evaluation.
- **Expansion:** The presenter mentions that I<sup>2</sup>C allows for the addition of more slave devices to the bus. The same process can be used to control multiple devices.
- **Conclusion:** The video concludes by emphasizing the importance of studying the **data sheet** of I<sup>2</sup>C devices for proper implementation. While I<sup>2</sup>C is useful, the video hints at other communication protocols like **SPI** and **one-wire interface**, which could be explored in future videos.

## Lesson-20:

### Thyristor Control:

- **Introduction:** The video introduces the **thyristor**, a controllable diode, and explores its functionality and applications. A thyristor can be turned on and off with a gate signal and stays on once triggered, unlike a regular diode. The presenter demonstrates how to use a thyristor for controlling power consumption in AC appliances, focusing on building a **phase angle control circuit**.
- **Thyristor Basics:**
  - A **diode** consists of two semiconductor layers, while a **thyristor** has four layers and includes an additional **gate** terminal.
  - The presenter uses a **TYN 604 thyristor** for demonstration. The basic operation involves applying a voltage to the gate to turn the thyristor on. Once turned on, it stays in a conductive state even if the gate signal is removed, until the current drops below a certain threshold (called **holding current**).
  - To turn off the thyristor, the current must be interrupted (e.g., using a MOSFET), though this is not ideal.
- **Practical Example:**
  - The presenter demonstrates the thyristor by using a small **LED** connected to the anode and cathode of the thyristor. When a positive voltage is applied to the gate, the LED lights up. However, the thyristor stays conductive once turned on, requiring a minimum current (**latching current**) to remain active.

- The thyristor shows a **turn-off time** (around **37 microseconds**) when no longer conductive, which can be tested by switching the **MOSFET** on and off rapidly.
- **AC Voltage:**
  - The presenter moves to demonstrate the thyristor with **AC voltage**. An **auto transformer** is used to step down mains voltage to safer levels (around 9V). However, in an AC system, the thyristor turns off automatically after each half-wave of the AC cycle, leading to incomplete control.
  - The issue is solved by using two thyristors in an **inverse parallel configuration**, forming a **triac**, which can control both halves of the AC cycle.
- **Phase Angle Control Circuit:**
  - The presenter designs a phase angle control circuit using a **microcontroller**. The process involves:
    - Using a **Full Bridge Rectifier** and **opto-coupler** to detect the zero-crossing points of the AC signal.
    - Using the zero-crossing signal to trigger a delay (between **0 and 10 milliseconds**) based on the **potentiometer** setting, controlling when the **triac** is triggered.
    - The circuit then controls the power sent to a light bulb.
- **Applications and Challenges:**
  - The phase angle control circuit can be used for controlling power to appliances like **heating elements** or adjusting the speed of motors in drills.
  - However, the method has a downside: **power factor degradation** due to the **non-sinusoidal** nature of the current, which is an area for further exploration.
- **Conclusion:**
  - The video wraps up by mentioning the **power factor** issue and encourages viewers to stay tuned for a more in-depth discussion in future videos.
  - The presenter asks viewers to like, share, and subscribe to the channel, and consider supporting through Patreon.

This type of circuit is useful for applications like **light dimming** or **motor speed control**, and the video provides a clear breakdown of how to design such circuits with thyristors.

## **Lesson-21:**

### **Operational Amplifier (Op-Amp) Video:**

- **Introduction:** The video explains **operational amplifiers (op-amps)**, their functions, and their importance in analog and digital electronics. Op-amps are commonly seen as **triangle-shaped components** in circuit schematics.
- **Op-Amp Basics:**
  - Op-amps come in **dual inline packages (DIP)** with different pin counts, often containing **one, two, or four op-amps**.
  - The **LM358 dual op-amp** is used for demonstration, powered by **0V (ground) and +12V**.
  - A **non-inverting amplifier** circuit is built using a voltage divider and feedback resistors, achieving an **amplification factor of 6.1**.
  - The **golden rule**: The **output** of an op-amp will adjust itself to maintain **zero voltage difference** between the inputs.
- **Amplification Example:**
  - An op-amp can amplify signals from sensors like **PT100 temperature sensors** or **electret microphones**.
  - When amplifying an **AC signal** from a microphone, **only the positive half-cycle is amplified**, requiring a **dual power supply (+/-12V)**.
  - **DC offset** can be used to make the op-amp function with a **single supply**, but this can cause **clipping** at high gains.
- **Op-Amp Imperfections:**
  - Real op-amps are not **ideal**:
    - They have **input impedance**, meaning some **current flows into the input**.
    - They have **output impedance**, limiting the **current they can supply**.
    - **Rail-to-rail op-amps** exist, allowing the output to reach the supply voltage.
- **Inverting Amplifier:**
  - A **better amplifier circuit** for microphones is an **inverting amplifier**, where:
    - The **non-inverting input (V+)** is **grounded**.
    - The **input signal goes through a resistor (R1)** to the **inverting input (V-)**.
    - A **feedback resistor (R2)** sets the **gain**.
    - **DC offset can be added** to allow single-supply operation.

- **Comparator Mode:**
  - When **no feedback** is used, the op-amp functions as a **comparator**:
    - If  $V_+ > V_-$ , the output jumps to **high voltage**.
    - If  $V_- > V_+$ , the output jumps to **low voltage**.
  - Dedicated **comparator ICs** offer **faster response times** than op-amps.
- **Applications of Op-Amps:**
  - Op-amps are used in **constant current sources, voltage followers, integrators, differentiators, summing amplifiers, Schmitt triggers**, and more.
- **Conclusion:**
  - The video emphasizes the **versatility of op-amps** and suggests more advanced topics for future videos.
  - The presenter encourages **liking, sharing, and subscribing**, as well as supporting the channel on **Patreon**.

### Note on Op-Amps

- **Op-amps** are versatile electronic components used for **signal amplification, filtering, and processing**.
- The **LM358 op-amp** is a **dual-package** op-amp that works with **a single power supply**.
- **Non-inverting amplifiers** provide positive gain, while **inverting amplifiers** offer better signal handling for AC inputs.
- **Op-amps can function as comparators**, switching between high and low output states based on input conditions.
- They are widely used in **sensor circuits, signal processing, and audio amplification**.

## Lesson-22:

### Operational amplifiers (op-amps) & BJT

Operational amplifiers (op-amps) are widely used components in analog and digital circuits. They typically come in dual inline packages with 8 to 14 pins, featuring one or more op-amps. The LM358 is a common dual op-amp IC.

Key points:

- **Non-inverting amplifier:** Uses a voltage divider to set gain, calculated as  $1 + (R_2/R_1)$ .

- **Inverting amplifier:** Uses a different configuration where the gain is  $- (R_2/R_1)$ .
- **Comparator mode:** Without feedback, the op-amp acts as a comparator, switching the output high or low based on input voltages.
- **Limitations:** Op-amps are not perfect; real ones have input currents, output impedance, and voltage limits.

Applications include sensor signal amplification (e.g., microphones) and active filters.

### **Summary of BJT as a Switch Video**

Bipolar Junction Transistors (BJTs) are semiconductor devices used for switching and amplification. They come in two types:

- **NPN (e.g., BC637):** Switches on when the base is given a positive voltage.
- **PNP (e.g., BD535):** Switches on when the base is grounded.

Key points:

- **Current gain ( $\beta$ )** determines how much base current controls the collector current.
- **Base resistor ( $R_b$ )** is crucial to limit current and prevent transistor damage.
- **Saturation voltage ( $V_{ce(sat)}$ )** causes power loss, making BJTs less efficient at high currents.
- **Darlington transistors (e.g., TIP142)** increase gain and allow low control currents but have higher power loss.

BJTs are commonly used in **power switches, LED drivers, and power regulation circuits**, but MOSFETs are often preferred for high-efficiency switching.

### **Notes**

- **Op-amps** are versatile, used for signal amplification, filtering, and voltage comparison.
- **BJTs** are simple and effective for low-power switching but inefficient at high currents.
- **Darlington transistors** allow small signals to control large currents but have drawbacks in efficiency.

## **Lesson-23:**

### **Summary of MOSFET as a Switch Video**

MOSFETs (Metal-Oxide-Semiconductor Field-Effect Transistors) are an efficient alternative to BJTs for switching applications. They offer **higher efficiency, lower power loss, and faster switching speeds**.

## Key Concepts:

- **Two main types:**
  - **N-Channel** (e.g., **IRLZ44N**): More commonly used. The source is connected to ground, and the load is between the drain and the supply voltage.
  - **P-Channel**: Works in reverse, where the source is at the supply voltage, and the load is connected to the drain.
- **Gate Voltage Control:**
  - Unlike BJTs, MOSFETs do not require a base current; they only need a high enough **gate-to-source voltage (Vgs)**.
  - For **logic-level MOSFETs**, 5V from an Arduino is sufficient to fully turn them on.
- **Pull-Down & Pull-Up Resistors:**
  - **N-Channel**: Uses a **10kΩ pull-down resistor** to prevent unwanted switching due to stray voltage.
  - **P-Channel**: Requires a **pull-up resistor** to work properly.
- **PWM Control for Dimming:**
  - Using an **Arduino PWM signal**, MOSFETs can efficiently control the brightness of an LED or motor speed.

## Challenges & Solutions:

- **Parasitic Capacitance & Oscillations:**
  - When switching high currents, **parasitic capacitance** can cause oscillations, leading to voltage spikes.
  - A **gate resistor (e.g., 470Ω)** slows the switching time, reducing unwanted oscillations.
- **High-Frequency Switching Issues:**
  - At high frequencies (e.g., **1 MHz**), **switching losses** increase due to repeated charging/discharging of the gate.
  - **MOSFET driver ICs** help by providing the necessary high-speed gate current.

## Advantages of MOSFETs over BJTs:

- Higher efficiency (~97%)
- Lower heat dissipation

- No need for continuous current at the gate
- Ideal for high-power applications

### **Final Notes:**

- **For low-power control** (e.g., LEDs, small motors), MOSFETs can be directly driven by an **Arduino**.
- **For high-power applications**, **gate drivers** are recommended for fast and efficient switching.
- **Oscillation and voltage spikes** must be managed using gate resistors and proper circuit design.

## **Lesson-24:**

### **Stepper Motor**

Stepper motors are commonly used in applications requiring **precise positioning**, such as **3D printers**. Unlike **brushed DC motors**, they rotate in discrete steps, allowing for **accurate control** of position and speed.

#### **Internal Structure of a Stepper Motor**

The video examines the **hybrid synchronous stepper motor**, which consists of:

**Rotor** – Permanent magnets arranged with alternating **North and South poles**.

**Pole Shoes** – Each has **50 teeth per sprocket**, slightly offset from one another.

**Stator** – Contains **8 physically separated coils**, but since there are only **4 wires**, they function as **2 coil pairs**.

By **applying current** to these coils in a specific sequence, the rotor moves in **precise steps**.

#### **How a Stepper Motor Works**

By energizing the coil pairs in a **specific order**, the rotor moves in **precise  $1.8^\circ$  steps** (200 steps per full rotation).

- **Black (VCC) & Green (GND)** → South Pole at  $0^\circ$
- **Blue (VCC) & Red (GND)** → North Pole at  $45^\circ$
- **Green (VCC) & Black (GND)** → South Pole at  $90^\circ$
- **Red (VCC) & Blue (GND)** → North Pole at  $135^\circ$

This cycle **repeats** continuously, causing the rotor to spin **accurately**.

#### **Stepper Motor Drivers & Control**

Manually switching coils is impractical, so **H-Bridge drivers** and **microcontrollers** (like Arduino) are used for control.

#### **H-Bridge Circuit:**

- Uses **N-channel & P-channel MOSFETs** to allow bidirectional current flow.
- Enables **precise control** of coil activation.

### **Microcontroller (Arduino) Control:**

- Sends signals to **MOSFET gates**, automating the stepping sequence.
- Can control **speed, direction, and number of steps**.  
**Stepper Motor Driving Methods**

**Wave Drive** – Activates only one coil at a time (low torque).

**Full-Step Drive** – Activates two coils simultaneously (higher torque).

**Half-Step Drive** – Alternates between one and two coils, doubling resolution (**400 steps per rotation**).

**Microstepping** – Uses **variable current** for ultra-smooth movement.

### **Microstepping with A4988 Driver IC**

Microstepping allows for **smoother rotation** and **quieter operation**. Instead of applying **constant voltage**, a **chopped PWM signal** is used to **control coil current**, creating a **sinusoidal waveform**.

- ◆ **555 Timer Circuit** generates a **variable frequency square wave**, triggering steps.
- ◆ **A4988 Driver IC** simplifies control, allowing microstepping down to **1/16 steps**.
- ◆ Microstepping **reduces noise and vibrations** while improving precision.  
**Advantages of Stepper Motors**

- **Precise control** – Can move **exact steps** without feedback.
- **High holding torque** – Maintains position when powered.
- **No need for encoders** – Unlike servos, positioning is inherent.
- **Microstepping reduces noise** – Smoother, quieter operation.

## **Lesson-25:**

### **Stepper Motor vs. Servo Motor – Working and Control**

#### **Stepper Motors**

- Commonly used for precise positioning tasks (e.g., 3D printers).
- **Structure:**
  - Contains a rotor with permanent magnets and stator coils.
  - Moves in discrete steps (e.g., 200 steps per rotation,  $1.8^\circ$  step angle).
- **Working Principle:**
  - Coils are energized in a specific sequence to rotate the rotor.
  - Different driving methods:

- **Wave Drive:** One coil is active at a time (low torque).
- **Full Step:** Two coils active simultaneously (higher torque).
- **Half Step & Microstepping:** Increases resolution and smoothness.
- **Control:**
  - H-bridge circuits switch the current direction.
  - Dedicated driver ICs (e.g., A4988) allow finer control (microstepping).
  - Microstepping reduces noise and makes movement smoother.

## Servo Motors

- Used in applications needing controlled angular movement (e.g., robotic arms).
- **Structure:**
  - Includes a DC motor, a gear system for torque increase, and a control circuit.
  - Uses a potentiometer for position feedback.
- **Working Principle:**
  - Position controlled using **PWM signals**:
    - 1 ms pulse → -90°
    - 1.5 ms pulse → 0°
    - 2 ms pulse → +90°
  - Control IC adjusts motor rotation based on feedback.
- **Control:**
  - Can be controlled via Arduino or simple circuits like a **555 timer**.
  - Modified servos can rotate **continuously** by removing the potentiometer and replacing it with resistors.

## Comparison

Feature	Stepper Motor	Servo Motor
<b>Control Type</b>	Open-loop (no feedback)	Closed-loop (feedback control)
<b>Precision</b>	High (fixed steps)	High (controlled via PWM)
<b>Holding Torque</b>	Yes (holds position when powered)	No (requires power to maintain position)

Feature	Stepper Motor	Servo Motor
<b>Rotation</b>	Infinite, precise steps	Typically 180° (modified for continuous rotation)
<b>Noise &amp; Smoothness</b>	Noisy, but microstepping improves it	Smoother movement

## Conclusion

- **Stepper motors** are best for precise, repeatable positioning.
- **Servos** are better for dynamic control with feedback.
- For applications needing smooth motion and speed control, **servos** are preferred.
- For high-precision, low-cost solutions, **stepper motors** are more practical.

## Lesson-26:

### Summary of 555 Timer IC Working and Applications

#### Introduction to 555 Timer IC

- One of the most widely used ICs in electronics.
- Can perform multiple functions in circuits by attaching external components.
- Contains **three 5KΩ resistors** forming a voltage divider, giving it its "**555**" name.

#### Internal Structure

- **Pin 1 (GND)**: Connected to ground.
- **Pin 8 (VCC)**: Power supply (typically 5V–15V).
- **Pin 2 (Trigger)**: Activates the IC when voltage drops below 1/3 of VCC.
- **Pin 6 (Threshold)**: Resets output when voltage exceeds 2/3 of VCC.
- **Pin 3 (Output)**: Provides high or low signal based on internal flip-flop.
- **Pin 7 (Discharge)**: Discharges external capacitor when needed.
- **Pin 4 (Reset)**: Can reset the IC when connected to ground.
- **Pin 5 (Control Voltage)**: Adjusts reference voltage for comparators (usually stabilized with a 10nF capacitor).

### 555 Timer Configurations

#### 1. Monostable Mode (One-Shot Pulse Generator)

- Generates a single pulse when triggered.

- **Working Principle:**
  - Initially, the capacitor is discharged.
  - Pressing a button triggers the timer, setting the output high.
  - The capacitor charges through a resistor.
  - When voltage reaches **2/3 VCC**, the output returns low, and the capacitor discharges.

- **Applications:**

- Delay circuits (e.g., notification lights).

## 2. Bistable Mode (Flip-Flop Circuit)

- Has **two stable states** (high and low).
- **Working Principle:**
  - **Pin 2 (Trigger)** acts as a **Set** input.
  - **Pin 4 (Reset)** acts as a **Reset** input.
  - Pressing one button turns the output ON, and pressing another turns it OFF.
- **Applications:**
  - Toggle switches, push-button latches.

## 3. Astable Mode (Oscillator Circuit)

- Generates a **continuous square wave** (oscillation).
- **Working Principle:**
  - The capacitor charges through **R1 and R2** and discharges through **R2**.
  - The ON-time depends on both **R1 and R2**, while the OFF-time depends only on **R2**.
- **Improvement:** Adding **two diodes** allows **separate control** of charge and discharge times.
- **Applications:**
  - LED blinking circuits, clock pulses, tone generators.

## PWM Generation Using 555 Timer

- A CMOS-based **555 Timer (TLC555)** provides **symmetrical** charge/discharge behavior.
- It achieves a **50% duty cycle** and adjustable frequency.

- Using **diodes and a potentiometer**, we can control the **duty cycle** for Pulse Width Modulation (PWM).
- **Applications:**
  - Motor speed control, dimming LEDs, power electronics.

### Key Takeaways

- The 555 timer is versatile, functioning as **a delay generator, pulse generator, or oscillator**.
- By adjusting **external resistors and capacitors**, different timing behaviors can be achieved.
- CMOS versions (e.g., **TLC555**) provide **better efficiency and lower power consumption**.
- The 555 timer is widely used in **timing circuits, frequency generators, and PWM control**.

## Lesson-27:

### Understanding ADC (Analog to Digital Converter) & Arduino

#### 1. Introduction to ADC:

- An **ADC (Analog to Digital Converter)** converts an analog voltage into a digital value.
- Arduino has a **10-bit ADC**, which means it can represent voltage levels in **1024 discrete steps** (from 0 to 1023).
- Example: A measured **3V analog input** might be converted to a digital value of **666** (if the reference voltage is 4.62V).

#### 2. Key Specifications of ADC:

- **Sampling Rate:** The number of samples taken per second.
  - Example: Arduino's default **sampling rate is 9 kHz**, meaning one sample every **112 microseconds**.
  - According to the **Nyquist Theorem**, the sampling rate should be **at least twice** the highest frequency of the signal for accurate reconstruction.
  - A **10x sampling rate** is preferred for better signal accuracy.
- **Resolution:** Determines the precision of the digital output.
  - **Higher bits = better accuracy.**
  - Example:

- 4-bit ADC → 312.5mV step size
- 10-bit Arduino ADC → 4.88mV step size
- 12-bit ADC (ADS7816) → 1.22mV step size

### 3. How ADC Works (Successive Approximation Method - SAR ADC):

- Components: Sample & Hold circuit, Comparator, DAC, and SAR (Successive Approximation Register).
- The process:
  1. Analog voltage is sampled and held steady.
  2. The DAC generates a reference voltage by setting the most significant bit (MSB).
  3. The Comparator checks if the input voltage is higher or lower than the DAC output.
  4. The SAR adjusts bits one by one until the final digital value is determined.

### 4. Using an External ADC (ADS7816) with Arduino:

- ADS7816 is a 12-bit ADC that offers better resolution.
- Connect it following the datasheet specifications, and use Arduino code to read values via SPI communication.

### 5. Flash ADC (Faster but Lower Resolution):

- Uses multiple comparators and a resistor voltage divider.
- Example: A 2-bit Flash ADC requires 4 comparators.
- Pros: Extremely fast.
- Cons: Requires many comparators, making higher-bit versions impractical (e.g., 8-bit Flash ADC needs 255 comparators).

### Conclusion:

- SAR ADCs (like in Arduino) offer a good balance of accuracy and speed.
- Flash ADCs are very fast but not practical for high resolution.
- External ADCs (e.g., ADS7816) can improve Arduino's precision.
- Understanding ADCs helps in signal processing and electronics applications.

## Lesson-28:

### MOSFET vs IGBT: Choosing the Right Switch for a Tesla Coil

## 1. Introduction

- While working on a **solid-state Tesla coil**, proper power management is essential.
- Common switching topologies: **Half-bridge** and **Full-bridge** circuits.
- Many Tesla coil circuits use **N-channel MOSFETs** in a **bootstrap full-bridge configuration**.
- However, some schematics use **IGBTs (Insulated Gate Bipolar Transistors)** instead of MOSFETs.
- The key question: **When should you use MOSFETs vs. IGBTs?**

## 2. Understanding IGBTs

- Like MOSFETs, **IGBTs have N-channel and P-channel types**, but P-channel is rarely used due to poor performance.
- IGBT structure combines a **MOSFET gate** with a **BJT output stage**.
- Example: **RGP50B60PD1 IGBT** (pins: **G - Gate, C - Collector, E - Emitter**).

## 3. Basic IGBT Switching Circuit

- **Emitter → Ground, Collector → Load → Supply Voltage.**
- Applying voltage to the **Gate** (above threshold) turns the IGBT **ON**.
- Increasing **Gate voltage** (up to 15V) reduces **collector-emitter voltage drop**, minimizing power losses.
- A **pull-down resistor (10kΩ)** is required to turn it **OFF** by discharging the Gate capacitance.

## 4. MOSFET vs. IGBT Switching Performance

- IGBTs behave like MOSFETs in terms of Gate control but have a **slower switching speed**.
- **MOSFETs switch faster** (e.g., 32 ns rise time vs. 145 ns for IGBT).
- **MOSFETs are preferred for high-frequency (>200 kHz) applications.**
- **IGBTs are better for medium-frequency (<200 kHz) and high-power applications.**

## 5. Power Loss Comparison

### Parameter    MOSFET    IGBT

Voltage Drop    0.024V    0.79V

Current Flow    1.7A    1.65A

## **Parameter    MOSFET IGBT**

Power Loss    0.04W      1.3W

- MOSFETs **maintain a lower voltage drop**, making them **more efficient** at low currents.
- IGBTs **handle higher voltages and currents but have higher conduction losses**.

## **6. Conclusion: When to Use What?**

- **MOSFETs:** Best for **high-frequency, low to medium power applications**.
- **IGBTs:** Ideal for **high voltage, high current, and medium-speed switching**.
- **For Tesla coils,** IGBTs can work if switching frequency is <200 kHz.

## **7. Final Thoughts**

- Understanding both **MOSFETs and IGBTs** is crucial for **power electronics**.
- For detailed explanations, refer to **MOSFET and BJT basics videos**.
- **Stay creative & keep experimenting!** 

# **Lesson-29:**

## **Summary of the Video on Solar Panels & Maximum Power Output**

### **1. Introduction to Solar Panels**

- Solar panels generate electricity when exposed to light.
- Larger panels produce more power.
- Understanding how to maximize power output is essential for applications like battery charging.

### **2. Solar Panel Structure**

- Made up of multiple **solar cells** connected in series to increase voltage.
- Each cell produces around **0.5V**, so a 100W panel with **36 cells** produces around **14.3V (open circuit voltage)**.
- Soldering individual cells is difficult due to their brittleness; buying pre-assembled panels is more practical.

### **3. Challenges in Series Connections**

- **Partial shading** (e.g., from clouds) increases resistance in affected cells, drastically reducing power output.

- **Bypass diodes** help by allowing current to flow around shaded cells, improving efficiency.
- **Blocking diodes** prevent reverse current flow when panels are connected in parallel.

#### 4. Understanding Power Output Variations

- **Standard Test Conditions (STC)** define rated panel power, but real-world efficiency is lower.
- Different loads (e.g., LEDs) affect output voltage due to the **internal resistance** of solar cells.
- Solar cells behave like **constant current sources**, with additional losses from semiconductor material defects and wiring.

#### 5. Finding the Maximum Power Point (MPP)

- By varying the load resistance, we can find the **optimal voltage and current combination** for maximum power extraction.
- The **Maximum Power Point (MPP)** is where the product of current and voltage is highest.
- **MPPT (Maximum Power Point Tracking) charge controllers** adjust the load to maintain optimal efficiency.
- **PWM charge controllers** are less efficient and can result in up to **40% power loss**.

#### 6. Conclusion

- Proper panel wiring, using bypass diodes, and choosing an **MPPT charge controller** significantly improve efficiency.
- Understanding how solar panels function helps in maximizing power output for practical use.

## Lesson-30

### Summary of the Video on Microcontroller Timers & PWM

#### 1. Importance of Timers in Microcontrollers

- Timers are essential for **precisely timed events** in projects like alarm clocks.
- Examples: Counting exactly 60 seconds before increasing the minute counter, blinking a display at a fixed rate, and controlling LED matrix animations.
- Used in generating **PWM signals** for sound alarms.

#### 2. Understanding Microcontroller Timers

- Found in different microcontrollers like **MSP430, PIC, and ATmega328P (Arduino Uno's microcontroller)**.
- Timers operate independently after initialization, freeing up the main program loop.
- **Timer 1** is a **16-bit timer** with multiple useful modes.

### 3. Issues with Traditional Delay-Based Timing

- Using `delay()` in Arduino **blocks execution**, causing the program to miss user inputs.
- Time accuracy drifts over long durations, leading to timing errors.

### 4. Normal Mode Operation

- In **Normal Mode**, the timer register counts from 0 to **65535** (16-bit max value).
- Once the maximum value is reached, the counter **overflows** and starts from 0 again.
- Overflow sets a **flag** that can trigger an **interrupt** (without blocking execution).

### 5. Using Prescalers to Adjust Timing

- Without a prescaler, overflow happens **every ~4 milliseconds** with a **16MHz clock**.
- Setting a **prescaler of 256** extends the overflow time to **1.04 seconds**, making it usable for event timing.
- A formula is used to adjust the **starting value** of the timer to get an **exact 1-second delay**.

### 6. Clear Timer on Compare Match (CTC) Mode

- Used to generate multiple interrupts at **specific intervals** (e.g., every 0.25s and 0.5s).
- In **CTC mode**, the timer resets when it matches a predefined value, rather than waiting for an overflow.
- Two **compare registers** (OCR1A & OCR1B) trigger **two independent interrupts**.

### 7. Generating PWM Signals with Timers

- **Fast PWM Mode** allows precise control of **duty cycle and frequency**.
- Uses an **8-bit counter**, so the timer counts from **0 to 255**.

- PWM output is generated on specific pins (Pin 9 & 10 for ATmega328P).
- The duty cycle is controlled by **OCR1A** and **OCR1B** registers.
- By adding a **prescaler of 1**, PWM frequency reaches **62.5kHz**.

## 8. Advanced PWM with Frequency Control

- By using the **ICR1 register**, the maximum counter value can be dynamically adjusted.
- This allows changing the **frequency up to 8 MHz**, while still controlling the duty cycle.

## 9. Conclusion

- Timers are powerful tools for **precise timing and PWM generation** in microcontrollers.
- Using interrupts instead of delay() improves **responsiveness**.
- Understanding timers allows **better control of electronics projects**.
- More details can be found in the **ATmega328P datasheet** (~100 pages on timers).

This summary covers the key concepts from the video for your notes. Let me know if you need further clarification! 